

<b>University of Ruse Angel Kanchev</b>			
<b>Department: Theoretical and measuring electrical engineering</b>			
<b>Course:</b>			
<b>Specialty:</b>			
<b>Student:</b>			<b>Fac. No:</b>
<b>Group:</b>	<b>Date:</b>	<b>Assistant:</b>	

## REPORT № 1

**Topic: Basic laws in electric circuits.**

**Task 1.** This task gives 4 points.

**Goal of the task:** .....

.....

.....

**Schematics of the experimental arrangement:**

<b>Quantity</b>	$U_{N0}, V$	$U_{N1}, V$	$U_{N2}, V$
<b>Value, V</b>	0		

Quantity	Value
$I_1, A$	
$I_2, A$	
$I_3, A$	
KCL with letters KCL with numbers	
$P_{E1}, W$	
$P_{R1}, W$	
$P_{R2}, W$	
$P_{R3}, W$	
Conservation of power with letters Conservation of power with numbers	

**Task 2.** This task gives 4 points.

**Goal of the task:** .....

.....

.....

**Schematics of the experimental arrangement:**

<b>Quantity</b>	$U_{N0}, V$	$U_{N1}, V$	$U_{N2}, V$	$U_{N3}, V$
<b>Value, V</b>	0			

<b>Quantity</b>	<b>Value</b>
$E_1, V$	
$U_{R1}, V$	
$U_{R2}, V$	
$U_{R3}, V$	
$U_{R4}, V$	
KVL for loop 1 with letters KVL for loop 1 with numbers	
KVL for loop 2 with letters KVL for loop 2 with numbers	
KVL for loop 3 with letters KVL for loop 3 with numbers	

**Conclusions:** This task gives 2 points.

.....

.....

.....