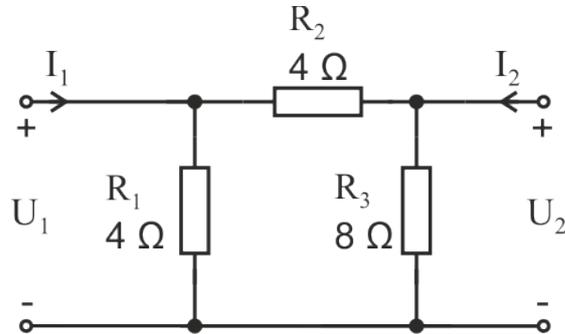


TWO-PORT NETWORKS ANALYSIS

Problem 1. Obtain the hybrid (H) parameters of the two-port.



The system with the H parameters is:

$$\begin{cases} \dot{U}_1 = H_{11} \dot{I}_1 + H_{12} \dot{U}_2 \\ \dot{I}_2 = H_{21} \dot{I}_1 + H_{22} \dot{U}_2 \end{cases}$$

In order to obtain them we need to analyze the circuit once for $I_1=0$ and once for $U_2=0$.

For $I_1=0$ the system of H equations becomes:

$$\begin{cases} U_1 = H_{11} I_1 + H_{12} U_2 \rightarrow U_1 = 0 + H_{12} U_2 \\ I_2 = H_{21} I_1 + H_{22} U_2 \rightarrow I_2 = 0 + H_{22} U_2 \end{cases}$$

Then two of the hybrid parameters are:

$$H_{12} = \frac{U_1}{U_2} \quad H_{22} = \frac{I_2}{U_2}$$


For $U_2=0$ the system becomes:

$$\begin{cases} U_1 = H_{11} I_1 + H_{12} U_2 \rightarrow U_1 = H_{11} I_1 + 0 \\ I_2 = H_{21} I_1 + H_{22} U_2 \rightarrow I_2 = H_{21} I_1 + 0 \end{cases}$$

and the other two parameters are:

$$H_{11} = \frac{U_1}{I_1} \quad H_{21} = \frac{I_2}{I_1}$$

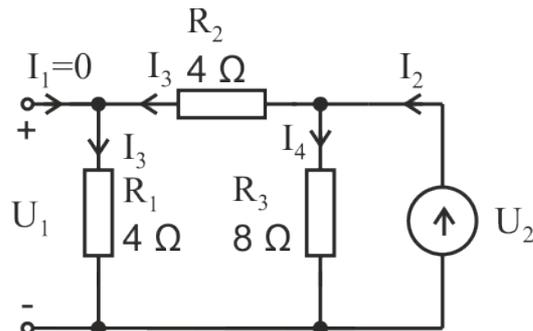Let us first examine the two port with an open circuit at the input ($I_1=0$), and power its output with a voltage source U_2 . The equivalent circuit is:



Tutorial exercise in Theory of Electrical Engineering. Two-port networks analysis.
 Author: Assoc. Prof. Dr. Boris Evstatiev, University of Ruse Angel Kanchev.

We need to obtain U_1 and I_2 (U_2 is already known). R_1 and R_2 are connected in series, so their equivalent resistance is:

$$R_{12} = R_1 + R_2 = 4 + 4 = 8 [\Omega]$$

R_{12} is connected in parallel to the ideal source U_2 so the current I_3 would be:

$$I_3 = \frac{U_2}{R_{12}} = \frac{U_2}{8}$$

Since U_1 is the voltage drop on R_1 we have:

$$U_1 = R_1 I_3 = 4 I_3 = 4 \frac{U_2}{8} = 0,5 U_2$$

The equivalent resistance of all resistors is:

$$R_{123} = \frac{R_{12} \cdot R_3}{R_{12} + R_3} = \frac{8 \cdot 8}{8 + 8} = 4 [\Omega]$$


Then the current I_2 is:

$$I_2 = \frac{U_2}{R_{123}} = 0,25 U_2$$

Now we can obtain two of the hybrid parameters:

$$H_{12} = \frac{U_1}{U_2} = \frac{0,5 U_2}{U_2} = 0,5 \qquad H_{22} = \frac{I_2}{U_2} = \frac{0,25 U_2}{U_2} = 0,25 [S]$$

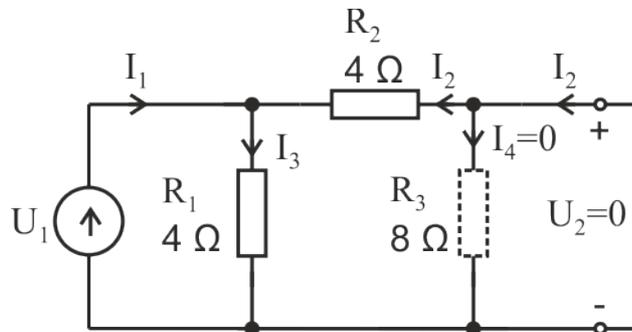Next we'll analyze the two-port with a short circuit at the output ($U_2 = 0$):



The voltage U_1 is known and we need to obtain I_1 and I_2 . The resistor R_3 is shunted by the short circuit, so in the circuit remain only R_1 and R_2 . We can write the following KVL equation:

$$U_1 = -R_2 \cdot I_2 \rightarrow U_1 = -4 I_2 \rightarrow I_2 = \frac{-1}{4} U_1 = -0,25 U_1$$

The equivalent resistance seen from the voltage source is:

$$R_{12} = \frac{R_1 \cdot R_2}{R_1 + R_2} = 2 [\Omega]$$

According to Ohm's law the current I_1 is:

Tutorial exercise in Theory of Electrical Engineering. Two-port networks analysis.
 Author: Assoc. Prof. Dr. Boris Evstatiev, University of Ruse Angel Kanchev.

$$I_1 = \frac{U_1}{R_{12}} = \frac{1}{2} U_1 = 0,5 U_1$$


Then the other two hybrid parameters are:

$$H_{11} = \frac{U_1}{I_1} = \frac{U_1}{0,5 U_1} = 2[\Omega] \quad H_{21} = \frac{I_2}{I_1} = \frac{-0,25 U_1}{0,5 U_1} = -0,5$$

and the H parameters of the two-port are:

$$H = \begin{bmatrix} 2[\Omega] & 0,5 \\ -0,5 & 0,25[S] \end{bmatrix}$$

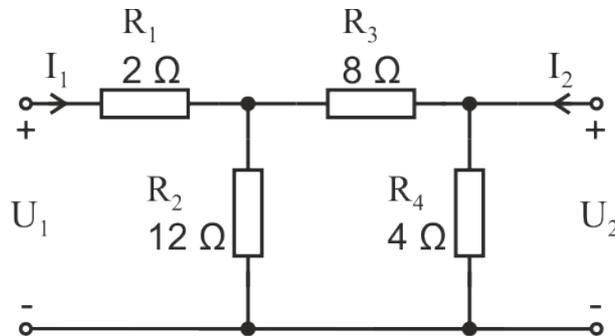Problem 2. Obtain the Z parameters of the two-port.



The system with the Z parameters is:

$$\begin{cases} \dot{U}_1 = Z_{11} \dot{I}_1 + Z_{12} \dot{I}_2 \\ \dot{U}_2 = Z_{21} \dot{I}_1 + Z_{22} \dot{I}_2 \end{cases}$$

So we need to solve the system for $I_1=0$ and for $I_2=0$.

For $I_1=0$ from the system with the Z parameters we obtain two of them:

$$U_1 = Z_{11} I_1 + Z_{12} I_2 = 0 + Z_{12} I_2 \quad \rightarrow \quad Z_{12} = \frac{U_1}{I_2}$$

$$U_2 = Z_{21} I_1 + Z_{22} I_2 = 0 + Z_{22} I_2 \quad \rightarrow \quad Z_{22} = \frac{U_2}{I_2}$$


For $I_2=0$ we obtain the other two parameters:

$$U_1 = Z_{11} I_1 + Z_{12} I_2 = Z_{11} I_1 + 0 \quad \rightarrow \quad Z_{11} = \frac{U_1}{I_1}$$

$$U_2 = Z_{21} I_1 + Z_{22} I_2 = Z_{21} I_1 + 0 \quad \rightarrow \quad Z_{21} = \frac{U_2}{I_1}$$

Let's first examine the two-port with an open circuit at the output ($I_2=0$) when the input is powered by a current source I_1 :

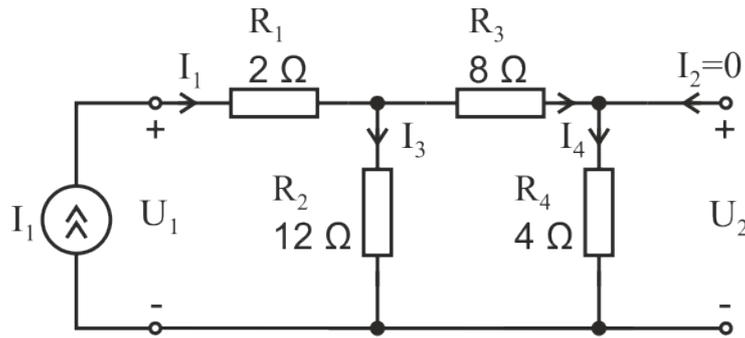Tutorial exercise in Theory of Electrical Engineering. Two-port networks analysis.
 Author: Assoc. Prof. Dr. Boris Evstatiev, University of Ruse Angel Kanchev.



We need to obtain U_1 and U_2 . The resistors R_3 and R_4 are connected in series and then in parallel to R_2 , so their equivalent resistance is:

$$R_{234} = \frac{R_2 \cdot (R_3 + R_4)}{R_2 + R_3 + R_4}$$

The voltage drop on R_{234} is:

$$U_{234} = I_1 R_{234} = I_1 \frac{R_2 \cdot (R_3 + R_4)}{R_2 + R_3 + R_4}$$

and the currents I_3 and I_4 are:

$$I_3 = \frac{U_{234}}{R_2} = I_1 \frac{R_2 \cdot (R_3 + R_4)}{R_2 + R_3 + R_4} \cdot \frac{1}{R_2} = I_1 \frac{8 + 4}{12 + 8 + 4} = 0,5 I_1$$

$$I_4 = \frac{U_{234}}{R_3 + R_4} = I_1 \frac{R_2 \cdot (R_3 + R_4)}{R_2 + R_3 + R_4} \cdot \frac{1}{(R_3 + R_4)} = I_1 \frac{12}{12 + 8 + 4} = 0,5 I_1$$

To obtain the voltages U_1 and U_2 we write two KVL equations:


$$U_1 = R_1 I_1 + R_2 I_3 = 2 I_1 + 12 I_3 = 2 I_1 + 12 \cdot 0,5 I_1 = 8 I_1$$

$$U_2 = R_4 I_4 = 4 I_4 = 4 \cdot 0,5 I_1 = 2 I_1$$

Then two of the Z parameters are:

$$Z_{11} = \frac{U_1}{I_1} = \frac{8 I_1}{I_1} = 8 [\Omega] \quad Z_{21} = \frac{U_2}{I_1} = \frac{2 I_1}{I_1} = 2 [\Omega]$$

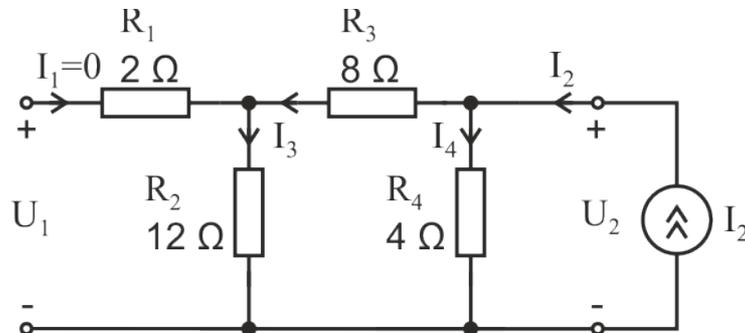Next we'll analyze the circuit for open circuit at the input ($I_1=0$) with a current source I_2 at the output:



Again we need to obtain U_1 and U_2 but this time we'll write a system of equations:

$$\begin{cases} I_2 = I_3 + I_4 \\ 0 = (8 + 12) I_3 - 4 I_4 \end{cases} \rightarrow \begin{bmatrix} I_3 \\ I_4 \end{bmatrix} \begin{bmatrix} 1 & 1 \\ 20 & -4 \end{bmatrix} = \begin{bmatrix} I_2 \\ 0 \end{bmatrix}$$

The determinants are:

$$\Delta = \begin{vmatrix} 1 & 1 \\ 20 & -4 \end{vmatrix} = -4 - 20 = -24$$

$$\Delta_3 = \begin{vmatrix} I_2 & 1 \\ 0 & -4 \end{vmatrix} = -4 I_2$$

$$\Delta_4 = \begin{vmatrix} 1 & I_2 \\ 20 & 0 \end{vmatrix} = -20 I_2$$

And the currents are:

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{-4 I_2}{-24} = 0,167 I_2$$

$$I_4 = \frac{\Delta_4}{\Delta} = \frac{-20 I_2}{-24} = 0,833 I_2$$

To obtain U_1 and U_2 we write 2 KVL equations:

$$U_1 = R_1 I_1 + R_2 I_3 = 2 I_1 + 12 I_3 = 0 + 12 \cdot 0,1667 I_2 = 2 I_2$$

$$U_2 = R_4 I_4 = 4 I_4 = 4 \cdot 0,8333 I_2 = 3,33 I_2$$


Now we can obtain the other two Z parameters:

$$Z_{12} = \frac{U_1}{I_2} = \frac{2 I_2}{I_2} = 2 [\Omega] \quad Z_{22} = \frac{U_2}{I_2} = \frac{3,33 I_2}{I_2} = 3,33 [\Omega]$$

To summer, the Z parameters of the two-port are:

$$Z = \begin{vmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{vmatrix} = \begin{vmatrix} 8 [\Omega] & 2 [\Omega] \\ 2 [\Omega] & 3,33 [\Omega] \end{vmatrix}$$

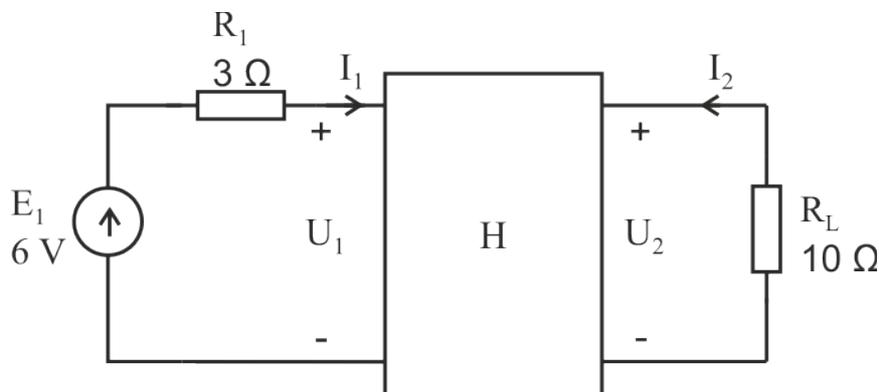Problem 3. Obtain the current and power of the load R_L , if the two-port is defined with its hybrid parameters: $H = \begin{bmatrix} 100 [\Omega] & 0,01 \\ 10 & 200 [mS] \end{bmatrix}$.



First we write a system of equations using Kirchoff's laws:

$$\begin{cases} 6 = 3 I_1 + U_1 \\ 0 = U_2 + 10 I_2 \end{cases}$$

We know that the system of hybrid equations is:

$$\begin{cases} \dot{U}_1 = H_{11} \dot{I}_1 + H_{12} \dot{U}_2 \\ \dot{I}_2 = H_{21} \dot{I}_1 + H_{22} \dot{U}_2 \end{cases} \rightarrow \begin{cases} U_1 = 100 I_1 + 0,01 U_2 \\ I_2 = 10 I_1 + 0,200 U_2 \end{cases}$$

We substitute the last equations in our system and obtain:

$$\begin{cases} 6 = 3 I_1 + U_1 \\ 0 = U_2 + 10 I_2 \end{cases} \rightarrow \begin{cases} 6 = 3 I_1 + 100 I_1 + 0,01 U_2 \\ 0 = U_2 + 10 (10 I_1 + 0,2 U_2) \end{cases} \rightarrow \begin{cases} 6 = 103 I_1 + 0,01 U_2 \\ 0 = 3 U_2 + 100 I_1 \end{cases}$$

In matrix form:

$$\begin{bmatrix} I_1 \\ U_2 \end{bmatrix} \begin{bmatrix} 103 & 0,01 \\ 100 & 3 \end{bmatrix} = \begin{bmatrix} 6 \\ 0 \end{bmatrix}$$

The determinants are:

$$\Delta = \begin{vmatrix} 103 & 0,01 \\ 100 & 3 \end{vmatrix} = 103 \cdot 3 - 100 \cdot 0,01 = 308$$

$$\Delta_2 = \begin{vmatrix} 103 & 6 \\ 100 & 0 \end{vmatrix} = 0 - 6 \cdot 100 = -600$$

Then the load voltage is:

$$U_2 = \frac{\Delta_2}{\Delta} = \frac{-600}{308} = -1,95 [V]$$


Finally the current and power of the load are:

$$0 = U_2 + 10 I_2 \rightarrow I_2 = \frac{-U_2}{R_T} = \frac{-(-1,95)}{10} = 195 [mA]$$

$$P_{RL} = U_2 (-I_2) = (-1,95) \cdot (-195 \cdot 10^{-3}) = 0,38 [W]$$

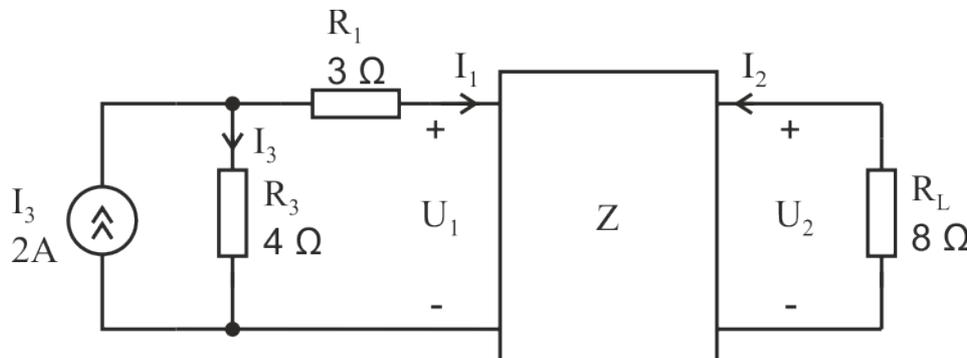Problem 4. Obtain the current and power of the load R_L , if the two-port is defined with its

Z parameters: $Z = \begin{bmatrix} 8[\Omega] & -3[\Omega] \\ -4[\Omega] & 9[\Omega] \end{bmatrix}$.



First we are going to write a system of equations:

Tutorial exercise in Theory of Electrical Engineering. Two-port networks analysis.
 Author: Assoc. Prof. Dr. Boris Evstatiev, University of Ruse Angel Kanchev.

$$\begin{cases} 2=I_1+I_3 \\ U_2=-8I_2 \\ U_1=4I_3-3I_1 \end{cases}$$

The system of Z equations is:

$$\begin{cases} \dot{U}_1=Z_{11}\dot{I}_1+Z_{12}\dot{I}_2 \\ \dot{U}_2=Z_{21}\dot{I}_1+Z_{22}\dot{I}_2 \end{cases} \rightarrow \begin{cases} U_1=8I_1-3I_2 \\ U_2=-4I_1+9I_2 \end{cases}$$

Then our system of Kirchoff's laws equations becomes:

$$\begin{cases} 2=I_1+I_3 \\ U_2=-8I_2 \\ U_1=4I_3-3I_1 \end{cases} \rightarrow \begin{cases} 2=I_1+I_3 \\ -4I_1+9I_2=-8I_2 \\ 8I_1-3I_2=4I_3-3I_1 \end{cases} \rightarrow \begin{cases} 2=I_1+I_3 \\ 0=4I_1-17I_2 \\ 0=3I_2+4I_3-11I_1 \end{cases}$$

In matrix form:

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \begin{bmatrix} 1 & 0 & 1 \\ 4 & -17 & 0 \\ -11 & 3 & 4 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ 0 \end{bmatrix}$$

The determinants are:

$$\Delta = \begin{vmatrix} 1 & 0 & 1 \\ 4 & -17 & 0 \\ -11 & 3 & 4 \end{vmatrix} = -68 + 12 - 187 = -234$$

$$\Delta_2 = \begin{vmatrix} 1 & 2 & 1 \\ 4 & 0 & 0 \\ -11 & 0 & 4 \end{vmatrix} = -32$$

Then the load current is:

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{-32}{-234} = 0,14[A],$$

and the power dissipated by the load is:

$$P_{RL} = I_2^2 R_T = 0,14^2 \cdot 8 = 0,15[W]$$