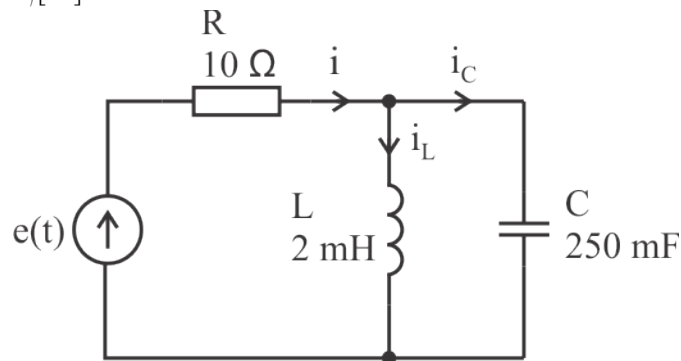


HOMework №3

Problem 1. Sketch the nonsinusoidal voltage $u(t)=17+3\sin\omega t[V]$ (5 points)


Problem 2. Sketch the nonsinusoidal current $i(t)=-10\sin\omega t+1\sin4\omega t[A]$ (5 points):

Problem 3. The circuit is powered by a nonsinusoidal voltage source $e(t)=10+2\sin(300t)[V]$:



- 1) For each of the harmonic components draw an equivalent circuit and estimate the current i (3+3 points);
- 2) Obtain the instantaneous current $i(t)$, its RMS value I and the power dissipated by the resistor R (4 points).

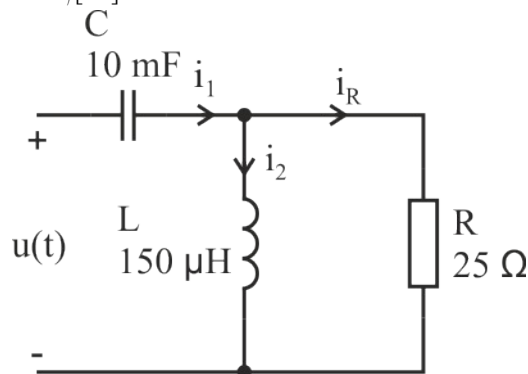Problem 4. The circuit is powered by a nonsinusoidal voltage source $u(t)=5\sin(100t)-3\sin(200t)[V]$:



- 1) For each of the harmonic components draw an equivalent circuit and estimate the current i_R (3+3 points);
- 2) Obtain the instantaneous current $i_R(t)$, its RMS value I_R and the power dissipated by the resistor R (4 points);