

SINUSOIDAL STEADY STATE CIRCUIT ANALYSIS

1. Introduction

A sinusoidal current has the following form:

$$i(t) = I_m \cdot \sin(\omega t + \varphi)$$

where I_m is the amplitude value;


$\omega = 2\pi f$ is the angular frequency;

φ is the phase shift.

Each sine could be represented with a phaser and a complex number:

$$i(t) = I_m \cdot \sin(\omega t + \varphi) \quad \rightarrow \quad \dot{I} = I_m \cdot e^{j\varphi} = I_m \cos(\varphi) + j I_m \sin(\varphi)$$

Let's consider a series RLC circuit:

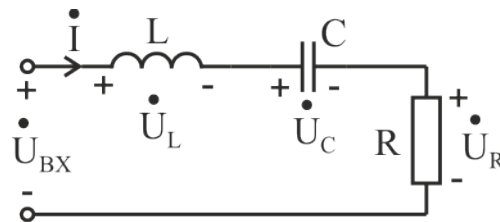

The KVL for the circuit is:

$$\dot{U}_{IN} = \dot{U}_R + \dot{U}_L + \dot{U}_C$$

where the voltage drops on the resistor, inductor and capacitor are:

$$\dot{U}_R = R \cdot \dot{I}$$

$$\dot{U}_L = j X_L \dot{I}$$

$$\dot{U}_C = -j X_C \dot{I}$$

X_L and X_C are the reactances of the inductor and the capacitor respectively:

$$X_L = \omega L \quad X_C = \frac{1}{\omega C}$$

Substituting the above equations in the KVL we obtain:

$$\dot{U}_{IN} = \dot{U}_R + \dot{U}_L + \dot{U}_C = \dot{I} (R + j(X_L - X_C)) = \dot{I} (R + jX)$$

where $Z = R + jX$ is the complex impedance of the circuit.

$$X = X_L - X_C = \omega L - \frac{1}{\omega C} \quad \text{is the total reactance of the branche.}$$

Every complex number could be presented in rectangular or exponential/polar form, so the complex impedance can also be written as:

$$Z = R + jX = z \cdot e^{j\varphi} = z \angle \varphi$$

where z is the magnitude of the impedance:

Tutorial exercise in Theory of Electrical Engineering. Sinusoidal steady state circuit analysis. Author: Assoc. Prof. Dr. Boris Evstatiev, University of Ruse Angel Kanchev.

$$z = \frac{U_{IN}}{I} = \sqrt{R^2 + X^2}$$

φ is the phase difference between the voltage and current in the branch:

$$\varphi = \operatorname{atan} \frac{X}{R}$$

2. Problems

Problem 1. Transform the sinusoids in complex form:

- $i_1(t) = 10 \sin(\omega t + 45^\circ) [A]$
- $i_2(t) = 12 \sin(\omega t - 90^\circ) [A]$
- $i_3(t) = 3 \sin(\omega t + 80^\circ) [A]$
- $u_1(t) = 100 \sin(\omega t) [V]$
- $u_2(t) = 50 \sin(\omega t - 35^\circ) [V]$

Solutions:

$$\dot{I}_1 = 10 e^{j45^\circ} [A]$$

$$\dot{I}_2 = 12 e^{-j90^\circ} [A]$$

$$\dot{I}_3 = 3 e^{j80^\circ} [A]$$

$$\dot{U}_1 = 100 e^{j0^\circ} = 100 [V]$$

$$\dot{U}_2 = 50 e^{-j35^\circ} [V]$$

Problem 2. Transform the phasors in sinusoidal form:

- $\dot{I}_1 = 2.25 e^{j30^\circ} [A]$
- $\dot{I}_2 = 1.5 e^{-j45^\circ} [A]$
- $\dot{U}_1 = 5 + j10 [V]$
- $\dot{U}_2 = -10 - j10 [V]$

Solutions:

$$i_1(t) = 2.25 \sin(\omega t + 30^\circ) [A]$$

$$i_2(t) = 1.5 \sin(\omega t - 45^\circ) [A]$$

$$\dot{U}_1 = 5 + j10 = \sqrt{5^2 + 10^2} e^{j \operatorname{arctg} \frac{10}{5}} = 11.2 e^{j63^\circ} \rightarrow u_1(t) = 11.2 \sin(\omega t + 63^\circ) [V]$$

$$\dot{U}_2 = -10 - j10 = -(10 + j10) = -\sqrt{(10)^2 + (10)^2} e^{j \operatorname{arctg} \frac{10}{10}} = -14.1 e^{j45^\circ}$$

$$\rightarrow u_2(t) = 14.1 \sin(\omega t + 45^\circ) [V]$$

Problem 3. Obtain the reactances of the inductors and capacitors:

- $L_1=10\text{mH}$ at frequency $f=50\text{ Hz}$
- $C_1=0,5\text{F}$ at frequency $f=110\text{ Hz}$
- $L_2=150\ \mu\text{H}$ at frequency $f=10\text{ kHz}$
- $L_3=150\ \mu\text{H}$ at frequency $f=100\text{ kHz}$
- $C_2=10\ \mu\text{F}$ at frequency $f=10\text{ kHz}$
- $C_3=10\ \mu\text{F}$ at frequency $f=100\text{ kHz}$

Solutions:

$$X_{L1}=\omega L_1=2\pi f L_1=2\pi \cdot 50 \cdot 10 \cdot 10^{-3}=3,14[\Omega]$$

$$X_{C1}=\frac{1}{\omega C_1}=\frac{1}{2\pi f C_1}=\frac{1}{2\pi \cdot 110 \cdot 0,5}=0,0029[\Omega]$$


$$X_{L2}=\omega L_2=2\pi f L_2=2\pi \cdot 10000 \cdot 150 \cdot 10^{-6}=9,42[\Omega]$$

$$X_{L3}=\omega L_3=2\pi f L_3=2\pi \cdot 100000 \cdot 150 \cdot 10^{-6}=94,2[\Omega]$$

$$X_{C2}=\frac{1}{\omega C_2}=\frac{1}{2\pi f C_2}=\frac{1}{2\pi \cdot 10000 \cdot 10 \cdot 10^{-6}}=1,6[\Omega]$$

$$X_{C3}=\frac{1}{\omega C_3}=\frac{1}{2\pi f C_3}=\frac{1}{2\pi \cdot 100000 \cdot 10 \cdot 10^{-6}}=0,16[\Omega]$$

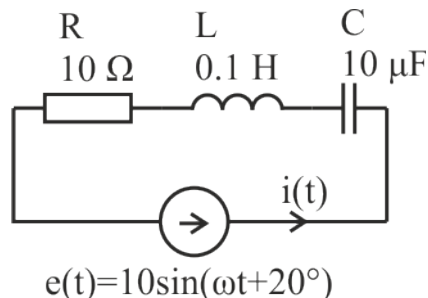Problem 4. Obtain the current $i(t)$ if the frequency of the source is $f=100\text{ Hz}$.



First we obtain the reactances of the reactive elements:

$$X_L=\omega L=2\pi f L=2\pi \cdot 100 \cdot 0,1=62[\Omega]$$


$$X_C=\frac{1}{\omega C}=\frac{1}{2\pi f C}=\frac{1}{2\pi \cdot 100 \cdot 10 \cdot 10^{-6}}=159[\Omega]$$

Next we present the sinusoidal source as phasor:

$$\dot{E}=10 e^{j20^\circ}[\text{V}]$$

Now we can draw an equivalent circuit with complex numbers:

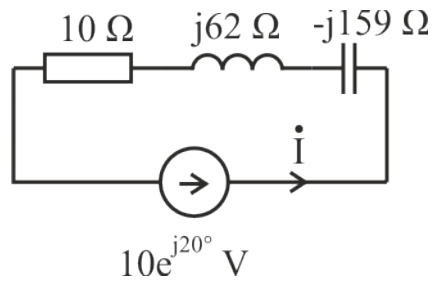Tutorial exercise in Theory of Electrical Engineering. Sinusoidal steady state circuit analysis. Author: Assoc. Prof. Dr. Boris Evstatiev, University of Ruse Angel Kanchev.




We write the KVL equation for the loop:

$$10e^{j20^\circ} = \dot{I}(10 + j60 - j159) \quad \rightarrow \quad \dot{I} = \frac{10e^{j20^\circ}}{97,5e^{-j84^\circ}} = 0,103e^{j104^\circ} [A]$$

Finally we transform the phasor in sinusoidal form:

$$\dot{I} = 0,103e^{j104^\circ} \quad \rightarrow \quad i(t) = 0,103 \sin(\omega t + 104^\circ) [A]$$

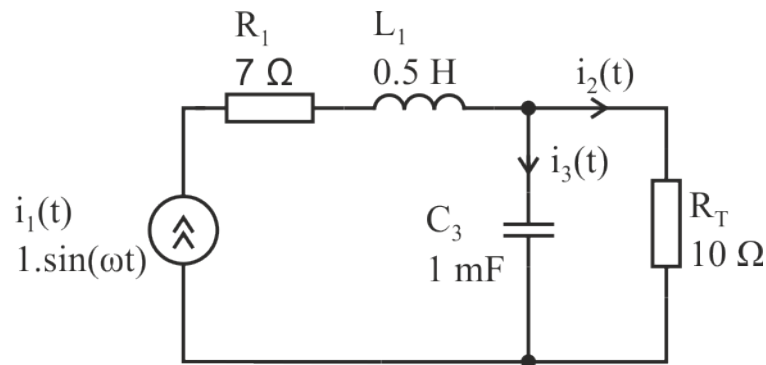Problem 5. Obtain the complex currents in the circuit if the frequency of the source is $f = 20 \text{ Hz}$ and obtain the active power, dissipated by the load R_T .



First we obtain the reactances:


$$X_{L1} = \omega L = 2\pi fL = 2\pi \cdot 20 \cdot 0,5 = 63 [\Omega]$$

$$X_{C3} = \frac{1}{\omega C} = \frac{1}{2\pi fC} = \frac{1}{2\pi \cdot 20 \cdot 1 \cdot 10^{-3}} = 8 [\Omega]$$

and present the sinusoidal source as phasor:

$$i_1(t) = 1 \cdot \sin(\omega t + 0) \quad \rightarrow \quad \dot{I}_1 = 1e^{j0} = 1 [A]$$

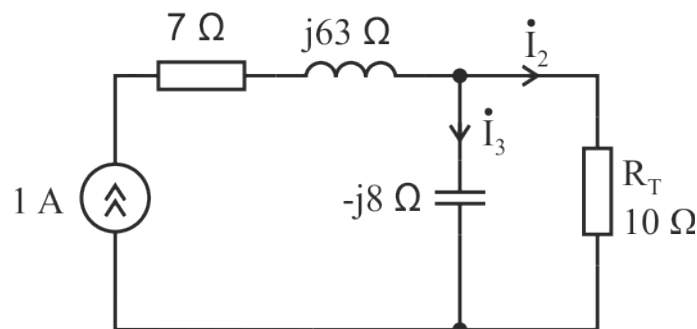Next we create an equivalent circuit with complex numbers:



For the circuit we can write two equations using Kirchoff's laws method:

Tutorial exercise in Theory of Electrical Engineering. Sinusoidal steady state circuit analysis. Author: Assoc. Prof. Dr. Boris Evstatiev, University of Ruse Angel Kanchev.

$$\begin{cases} 1 = \dot{I}_2 + \dot{I}_3 \\ 0 = 10\dot{I}_2 + j8\dot{I}_3 \end{cases} \rightarrow \begin{bmatrix} \dot{I}_2 \\ \dot{I}_3 \end{bmatrix} \begin{bmatrix} 1 & 1 \\ 10 & j8 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

The determinants are:

$$\Delta = \begin{vmatrix} 1 & 1 \\ 10 & j8 \end{vmatrix} = 1 \cdot j8 - 10 = -10 + j8$$

$$\Delta_2 = \begin{vmatrix} 1 & 1 \\ 0 & j8 \end{vmatrix} = j8$$

$$\Delta_3 = \begin{vmatrix} 1 & 1 \\ 10 & 0 \end{vmatrix} = -10$$

Then the complex currents are:

$$\dot{I}_2 = \frac{\Delta_2}{\Delta} = \frac{j8}{-10 + j8} = \frac{8 e^{j90^\circ}}{12,8 e^{-j39^\circ}} = 0,63 e^{j129^\circ} [A]$$

$$\dot{I}_3 = \frac{\Delta_3}{\Delta} = \frac{-10}{-10 + j8} = \frac{-10}{12,8 e^{-j39^\circ}} = 0,78 e^{j39^\circ} [A]$$

The corresponding sinusoidal currents are:


$$\dot{I}_2 = 0,63 e^{j129^\circ} \rightarrow i_2(t) = 0,63 \sin(\omega t + 129^\circ) [A]$$

$$\dot{I}_3 = 0,78 e^{j39^\circ} \rightarrow i_3(t) = 0,78 \sin(\omega t + 39^\circ) [A]$$

Finally the dissipated power by the load R_T is:

$$P = \left(\frac{I_{2m}}{\sqrt{2}} \right)^2 R_T = \left(\frac{0,63}{\sqrt{2}} \right)^2 10 = 1,98 [W]$$

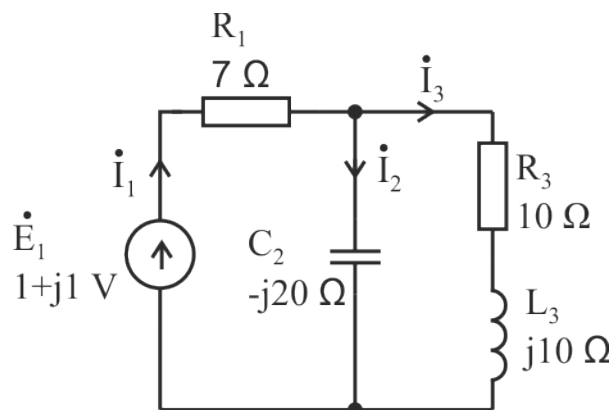Problem 6. Obtain the currents in the circuit and the powers of R_3 and L_3 .



We'll use nodal analysis. There are two nodes, so we let $\dot{U}_0 = 0$ and need 1 equation:

$$\dot{I}_1 = \dot{I}_2 + \dot{I}_3 \rightarrow \frac{\dot{U}_0 - \dot{U}_1 + 1 + j1}{7} = \frac{\dot{U}_1 - \dot{U}_0}{-j20} + \frac{\dot{U}_1 - \dot{U}_0}{10 + j10}$$

Tutorial exercise in Theory of Electrical Engineering. Sinusoidal steady state circuit analysis. Author: Assoc. Prof. Dr. Boris Evstatiev, University of Ruse Angel Kanchev.

$$0,14 + j0,14 - 0,14 \dot{U}_1 = j0,05 \dot{U}_1 + 0,05 \dot{U}_1 - j0,05 \dot{U}_1 \quad \rightarrow \quad 0,14 + j0,14 = 0,19 \dot{U}_1$$

$$\dot{U}_1 = 0,74 + j0,74$$

Then our currents are:

$$\dot{I}_1 = 0,14 + j0,14 - 0,14 \dot{U}_1 = 0,05 \cdot e^{j45^\circ} \text{ [A]}$$

$$\dot{I}_2 = j0,05 \dot{U}_1 = j0,05(0,74 + j0,74) = 0,05 \cdot e^{j135^\circ} \text{ [A]}$$

$$\dot{I}_3 = (0,05 - j0,05) \dot{U}_1 = (0,05 - j0,05)(0,74 + j0,74) = 0,07 \text{ [A]}$$


The power dissipated in R_3 is active:

$$P_{R3} = \left(\frac{I_{3m}}{\sqrt{2}} \right)^2 \cdot R_3 = \left(\frac{0,07}{\sqrt{2}} \right)^2 \cdot 10 = 0,025 \text{ [W]}$$

The power of the inductor is purely reactive:

$$Q_{L3} = \left(\frac{I_{3m}}{\sqrt{2}} \right)^2 \cdot X_{L3} = \left(\frac{0,07}{\sqrt{2}} \right)^2 \cdot 10 = 0,025 \text{ [VAR]}$$

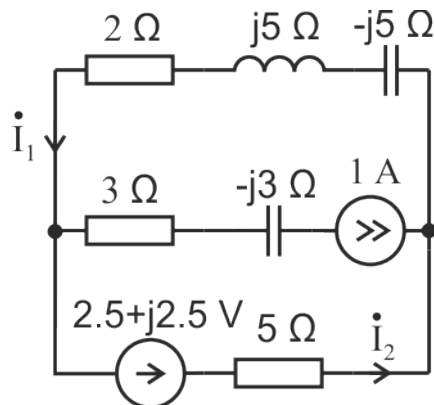Problem 7. Obtain the complex currents in the circuit.



The circuit has 2 unknown currents so we need 2 equations (using Kirchoff's laws):

$$\begin{cases} 1 + \dot{I}_2 = \dot{I}_1 \\ 2,5 + j2,5 = 5\dot{I}_2 + \dot{I}_1(2 + j5 - 5j) \end{cases}$$

In matrix form:

$$\begin{bmatrix} \dot{I}_1 \\ \dot{I}_2 \end{bmatrix} \begin{bmatrix} 1 & -1 \\ 2 & 5 \end{bmatrix} = \begin{bmatrix} 1 \\ 2,5 + j2,5 \end{bmatrix}$$

The determinants are:

$$\Delta = \begin{vmatrix} 1 & -1 \\ 2 & 5 \end{vmatrix} = 1 \cdot 5 - (-2) = 7$$

Tutorial exercise in Theory of Electrical Engineering. Sinusoidal steady state circuit analysis. Author: Assoc. Prof. Dr. Boris Evstatiev, University of Ruse Angel Kanchev.

$$\Delta_1 = \begin{bmatrix} 1 & -1 \\ 2,5+j2,5 & 5 \end{bmatrix} = 5+2,5+j2,5 = 7,5+j2,5$$

$$\Delta_2 = \begin{bmatrix} 1 & 1 \\ 2 & 2,5+j2,5 \end{bmatrix} = 2,5+j2,5-2 = 0,5+j2,5$$

Then the complex currents are:

$$\dot{I}_1 = \frac{\Delta_1}{\Delta} = \frac{7,5+j2,5}{7} = 1,07+j0,36 = 1,13 e^{j18,6^\circ} [A]$$

$$\dot{I}_2 = \frac{\Delta_2}{\Delta} = \frac{0,5+j2,5}{7} = 0,07+j0,36 = 0,37 e^{j79^\circ} [A]$$