

LABORATORY EXERCISE 3

Mutually coupled inductors.

Goal of the lab: To demonstrate the energy transfer between mutually coupled inductors and the creation of equivalent circuit without mutual induction.

1. Required equipment

Equipment	Count
Breadboard	1 pc.
A set of connecting wires	1 pc.
Function generator	1 pc.
Two channel oscilloscope	1 pc.
Inductor 290 μH	2 pc.
Resistor 100 Ω , 5 W	1 pc.
Resistor 150 Ω , 5 W	1 pc.

2. Tasks

Task 1. Obtain the self inductance of the two inductors.

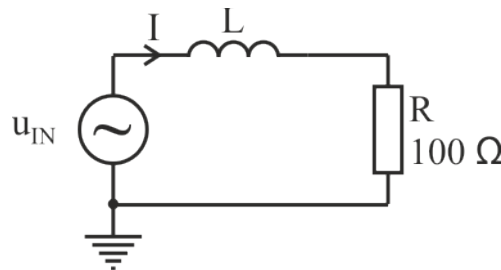


Fig. 1.

Step 1. Connect the circuit in fig. 1 on the breadboard. With the oscilloscope probes observe the input voltage $u_{\text{IN}}(t)$ and the resistor voltage drop $u_{\text{R}}(t)$.

Step 2. Power the circuit from the function generator with sinusoidal voltage $U_{\text{IN}}=6\text{V}_{\text{pp}}$ with frequency $f=80\text{kHz}$.

Step 3. Obtain the amplitudes U_{IN} and U_{R} of the observed sines.

Step 4. Estimate the amplitude of the voltage drop on the coil:

$$U_L = \sqrt{U_{\text{IN}}^2 - U_{\text{R}}^2}$$

Step 5. Obtain the current amplitude according to Ohm's law:

$$I = \frac{U_{\text{R}}}{R}$$

Step 6. Obtain the reactance of the coil:

$$X_L \cdot I = U_L \quad \rightarrow \quad X_L = \frac{U_L}{I}$$

Step 7. Obtain the self inductance of the coil:

$$X_L = \omega L \quad \rightarrow \quad L = \frac{X_L}{\omega} = \frac{X_L}{2 \cdot \pi \cdot f}$$

Step 8. Repeat steps 1-7 for the second coil.

Task 2. Obtain the coefficient of mutual inductance M between the two coils from problem 1, if they are closely adjoined.

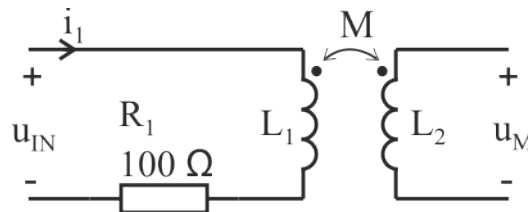


Fig. 2.

Step 1. Connect the circuit in fig. 2 on the breadboard and power it with sinusoidal voltage $U_{IN} = 6V_{pp}$ with frequency $f = 80kHz$.

Step 2. Connect the oscilloscope probes to observe the input voltage u_{IN} and the resistor voltage u_{R1} . Obtain their amplitudes U_{IN} и U_{R1} .

Step 3. Connect the second probe to the secondary coil L_2 and obtain the amplitude of the induced voltage U_M .

Step 4. Estimate the amplitude of the current I_1 according to Ohm's law:

$$I_1 = \frac{U_{R1}}{R_1}$$

Step 5. Obtain the resistance from mutual inductance:

$$U_M = I_1 \cdot X_M \quad \rightarrow \quad X_M = \frac{U_M}{I_1}$$

Step 6. Obtain the mutual inductance:

$$X_M = \omega \cdot M \quad \rightarrow \quad M = \frac{X_M}{\omega} = \frac{X_M}{2 \cdot \pi \cdot f}$$

Step 7. Obtain the coupling coefficient between the coils:

$$k = \frac{M}{\sqrt{L_1 \cdot L_2}}$$

Step 8. Experiment with the mutually coupled inductors and observe the changes in the induced voltage $u_M(t)$ when changing the distance and disposition of the two coils.

Task 3. Obtain the amplitude of the current i_2 through the load R_L .

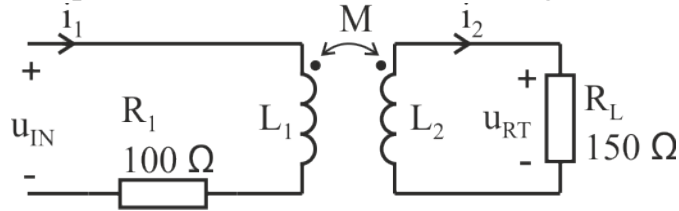


Fig. 3.

Step 1. Modify the circuit from the previous task with a load $R_L=150\Omega$, as shown in fig. 3 and measure the amplitude U_{RL} of the voltage drop on R_L .

Step 2. Obtain the amplitude of the current $i_2(t)$ according to Ohm's law:

$$I_2 = \frac{U_{RL}}{R_L}$$

Step 3 (homework). Analyze the circuit in fig. 3 and obtain the amplitude of the current I_2 (Assume the input voltage is $u_{IN}=3.\sin(\omega t)$ [V] (zero time shift) with frequency $f=80\text{kHz}$).

- Obtain the reactances of the inductors and the mutual reactance:

$$X_{L1} = \omega L_1 = \dots$$

$$X_{L2} = \omega L_2 = \dots$$

$$X_M = \omega M = \dots$$

- Create an equivalent circuit without mutual inductance (fig. 4).

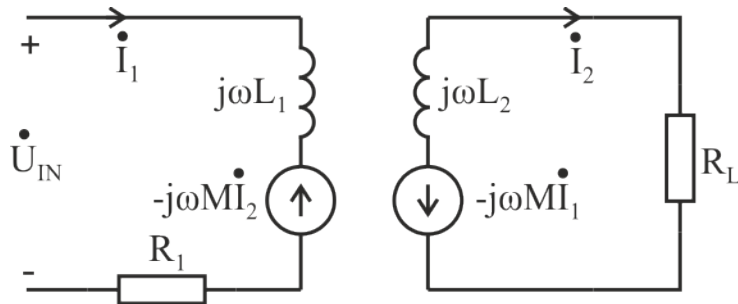


Fig. 4.

- Solve the circuit and obtain the phasor \dot{I}_2 and its amplitude I_2 .

3. Questions

1. What is the meaning of the self inductance and the coupling coefficients?
2. Can you explain the procedure to experimentally obtain the two coefficients?
3. How does the induced voltage drop change when the distance and disposition between the two coils changes?
4. Does the estimated current from task 3 match the experimental one? Why?
5. Does the voltage drop on L_2 change after loading with R_T ? Why?